

Project 1

Due Friday, October 10, 6:00pm, submitted to Canvas.

Submission: Prepare a concise report (< 5 pages) with important results only. You don't have to include the entire set of your circuit schematics or layout plots. Place the report in Assignment at Canvas with the filename as: EE5323_Project_1_your name.

The objective of this software lab is to exercise SPICE circuit simulations with Cadence tools. The technology used in this course is TSMC 16nm. $V_{DD}=0.8V$.

0. SPICE startup

Get familiar with the tools and the simulation environment. No submission needed for this problem.

1. Technology characteristics

Figure 1 shows a single NMOS and PMOS. In this problem, we calibrate the IV characteristics of this 16nm technology. Each transistor has 8 fins.

 


Figure 1. Single transistors

- a. For the NMOS,
 - (1) Plot out I_{DS} vs. V_{DS} in one figure, for $V_{GS}=0.05V-V_{DD}$, at the step size of **150mV**; $V_{DS}=0-V_{DD}$, at the step size of 1mV;
 - (2) Plot out $\log(I_{DS})$ vs. V_{GS} , for $V_{DS}=0.15V$ and V_{DD} ; $V_{GS}=0-V_{DD}$, at the step size of 1mV.

- b. Repeat Step (1) for the PMOS transistor.

2. CMOS inverter design

Figure 2 shows the design of a CMOS inverter. Both PMOS and NMOS FinFETs have 8 fins. **$C_L=10fF$, which is added in the test bench, not in the schematic.**

 


Figure 2. The schematics of a CMOS inverter

- a. Plot out the voltage transfer characteristic (VTC), which is the curve of V_{out} vs. V_{in} , when V_{in} sweeps from 0 to V_{DD} .
- b. Apply a ramp input to V_{in} , which is a 0 to V_{DD} switching, with the transition time $T_r=20ps$ (as shown in Figure 2). Plot out the waveform of V_{out} . Measure the 50% V_{DD} delay (i.e., time difference from the 50% point of input to the 50% point of output) and the time for V_{out} to transit from 90%-10% V_{DD} .

3. A NMOS only inverter

 


Figure 3. A NMOS only inverter

Figure 3 shows the design of an inverter with NMOS only. Both NMOS transistors have 8 fins.

- Simulate the maximum and minimum voltages at V_{out} . What's the corresponding V_{in} for them?
- Similar to a. in Prob. 2, plot out the VTC.
- Compare this design with the CMOS inverter. What are the main disadvantages?